

Instruction:

Complete all questions in **1 hour**.

- Draw the logic diagram of the following gates using logsim and complete the

Truth tables.

a. AND

A	B	A.B
0	0	0
0	1	0
1	0	0
1	1	1

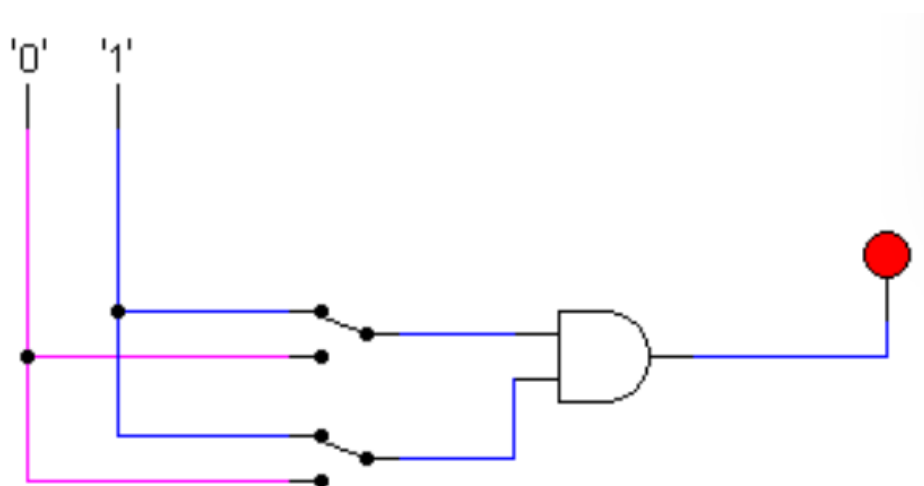


Fig 1:AND GATE

Prepared by:Aman kumar sah

b. NOR (do the same as in Q No a for all of the following)

A	B	$(A+B)'$
0	0	1
0	1	0
1	0	0
1	1	0

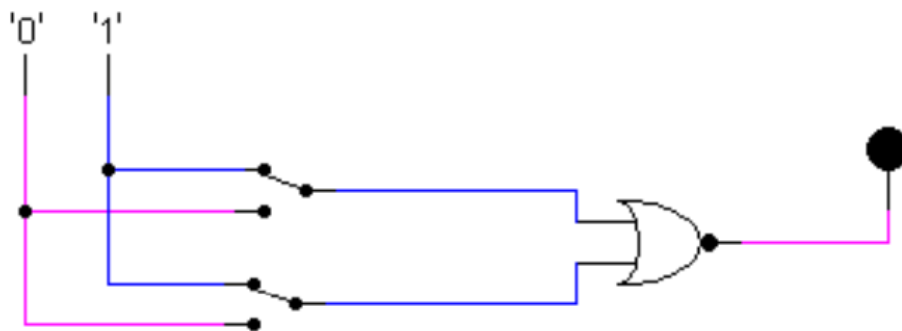


fig 2:NOR GATE

Prepared by:Aman Kumar Sah

c. OR

A	B	(A+B)
0	0	0
0	1	1
1	0	1
1	1	1

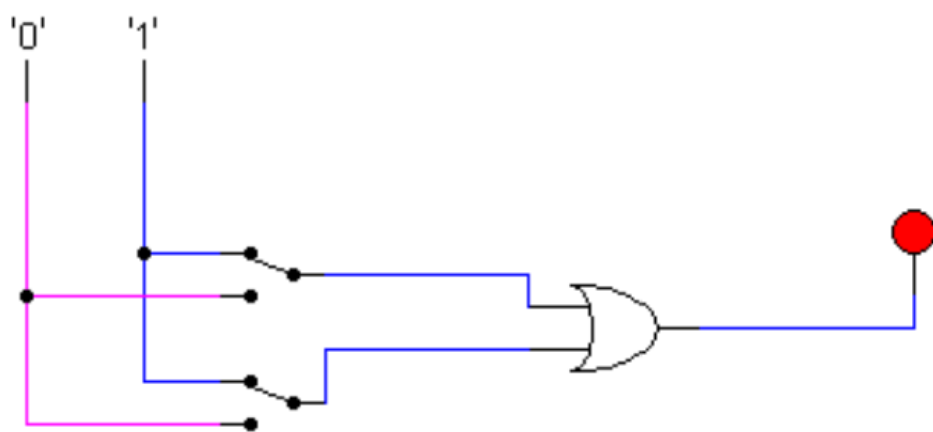


Fig:OR GATE
Prepared By:Aman Kumar Sah

d. NAND (using NOT and AND)

A	B	(A.B)'
0	0	1
0	1	1
1	0	1

1	1	0
---	---	---

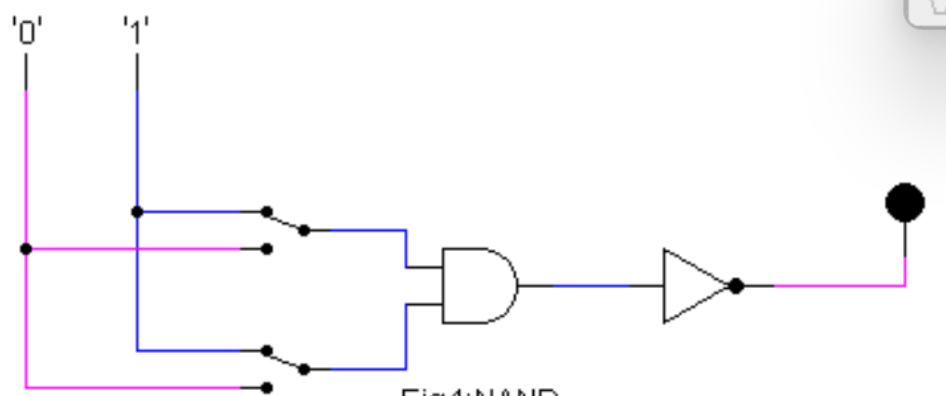


Fig4:NAND

Prepared By:Aman Kumar Sah

e. XOR using AOI

A	B	$AB' + A'B$
0	0	0
0	1	1
1	0	1
1	1	0

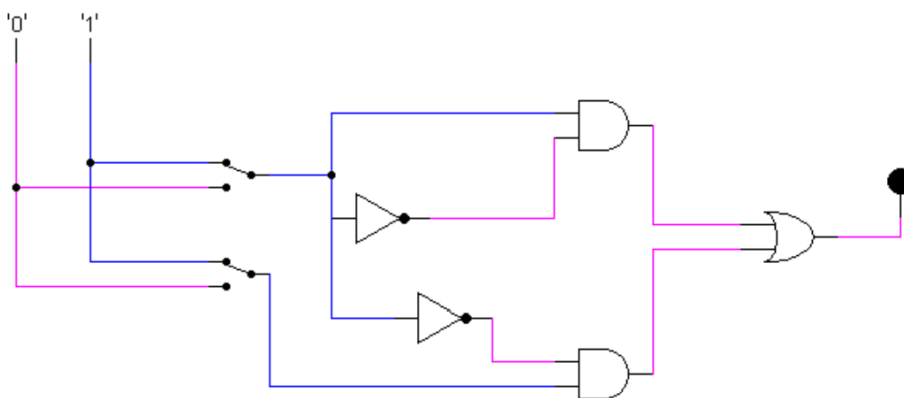


Fig 5:XOR

Prepared By:Aman Kumar Sah

2. Use LogSim to build the equivalent circuit for the following Boolean equations.

Prove that the expressions are equivalent by computing truth table.

$$(A+B)' = A' \cdot B'$$

A	B	$(A+B)'$	$A' \cdot B'$
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0

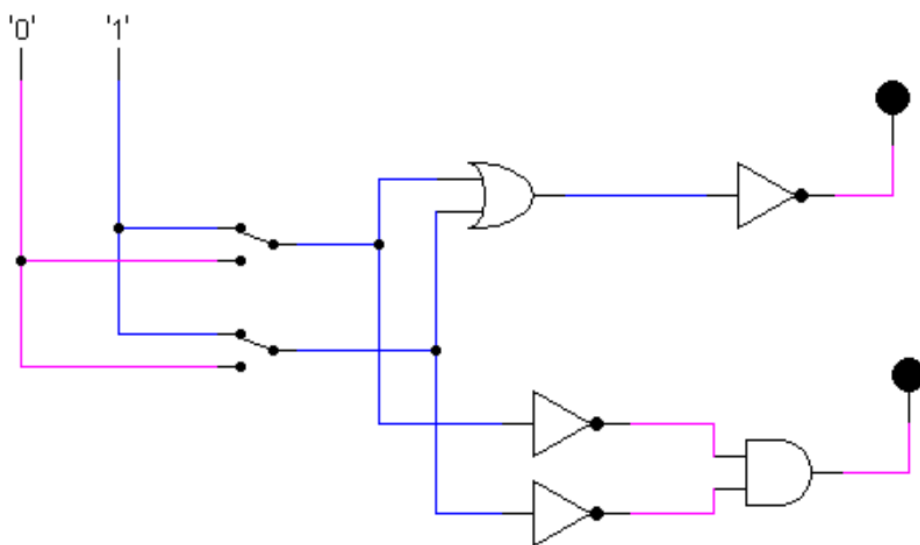


Fig 6
Prepared By: Aman kumar Sah

3. Draw the following circuit of half adder using LogSim.

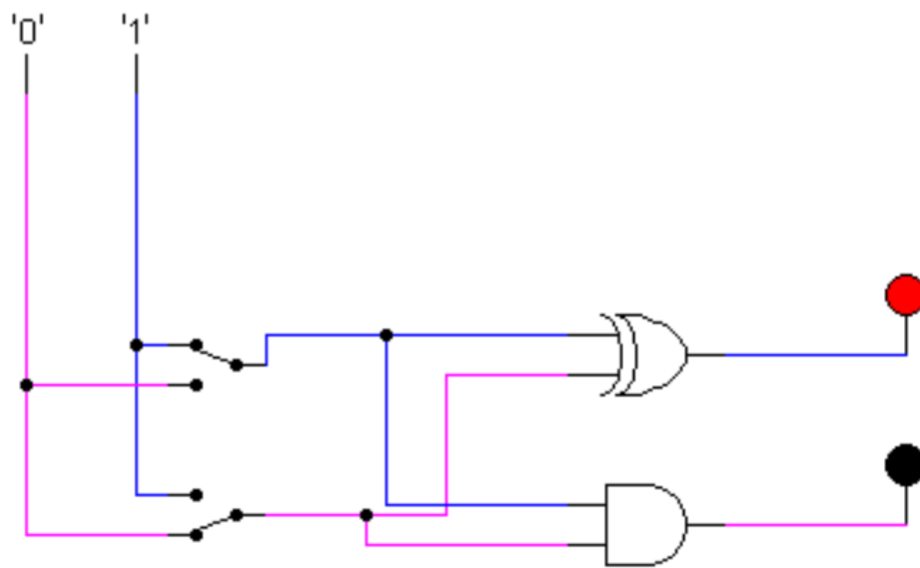


Fig:7

Prepared By:Aman Kumar Sah

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

4. Draw full adder using Logsim and construct truth table.

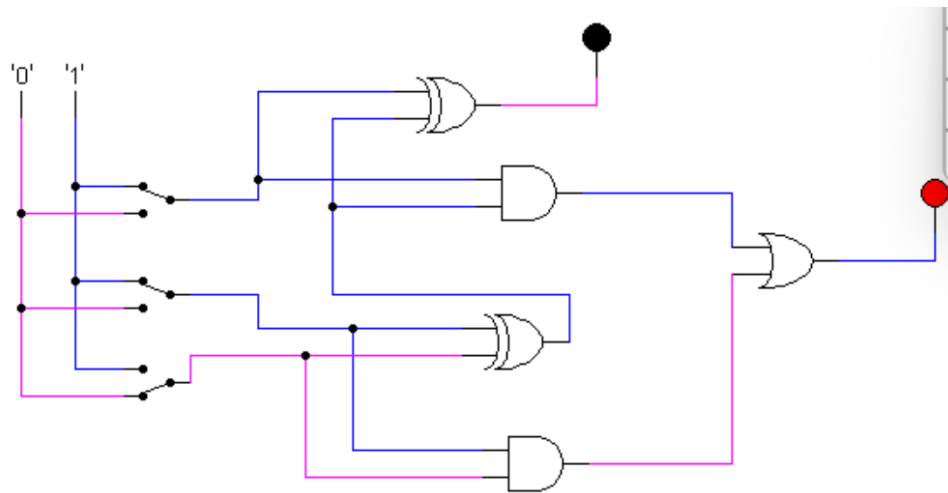


Fig:Full adder
Prepared By:Aman Kumar Sah

A	B	C	Sum	Carry out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

5.Draw the logic circuit for the following Boolean equations using logsim simulator.

- $AB+C$

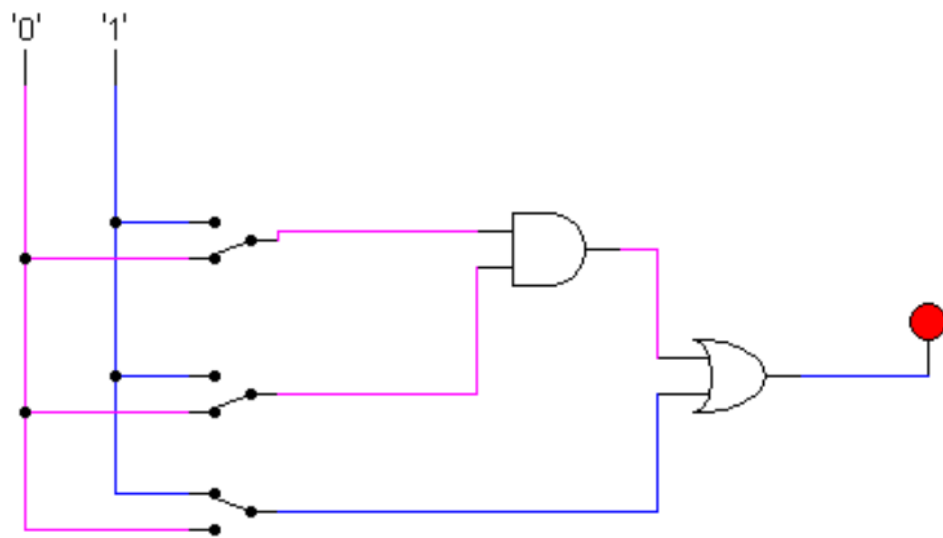


Fig 5.1

Prepared By:Aman Kumar Sah

- $A(B+C)$

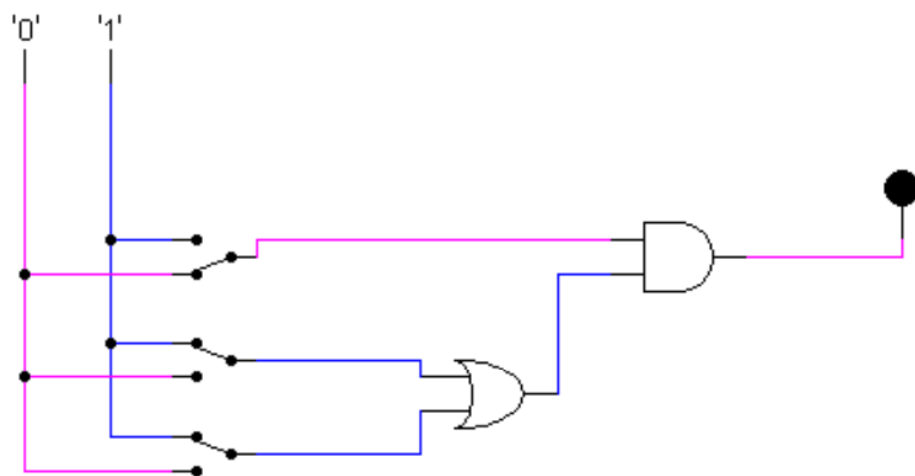


Fig 5.2

Prepared By:Aman Kumar Sah

- $X'Y'Z'$

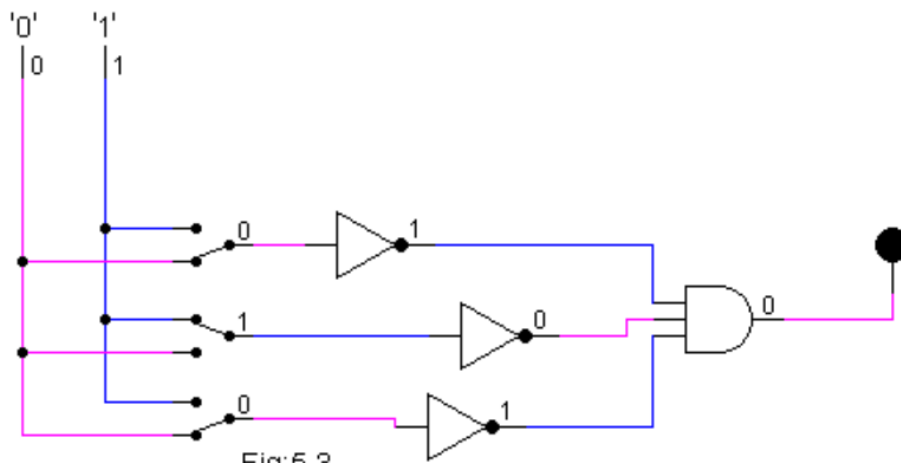


Fig:5.3
Prepared By:Aman Kumar Sah